

# Fundamentals of CMOS Design II

Ronald Valenzuela

[ronald.valenzuela@synopsys.com](mailto:ronald.valenzuela@synopsys.com)

Corporate Application Engineer - Synopsys

# Outline


Gate Performance

Gate Power


System Analysis

# Gate Performance

# We want to build Chips


 


0011100110011

 

## To perform complex binary calculations

 
 
# But what we are really are building CIRCUITS



## And circuits have transient response



# Pull Up Delay

- Rise time calculation

  

# Pull Down Delay


- Fall time calculation

  
 
# Delay - And then...


$$H(s) = \frac{1}{1 + sRC} \quad \Rightarrow \quad V_{out} = V_{dd}(1 - e^{\frac{-t}{R_P C}})$$

- Propagation delay is the time when when  $V_{out}$  reaches  $\frac{1}{2} V_{dd}$
- $t_{pd} = RC * \ln 2 = 0.69 * RC$
- So simple that we will take this value as the delay for hand calculations.
- Define gate delay as:  
Time from input crossing  $V_{dd}/2$  to output crossing  $V_{dd}/2$  and approximate to  $RC$





 Unfortunately, we don't always have a 1st order system




$$H(s) = \frac{1}{1 + s(R_1C_1 + (R_1 + R_2)C_2) + s^2R_1C_1R_2C_2}$$

This is too complex. It defeats the purpose of simplifying a CMOS circuit into an equivalent RC network

**Need something simpler!**



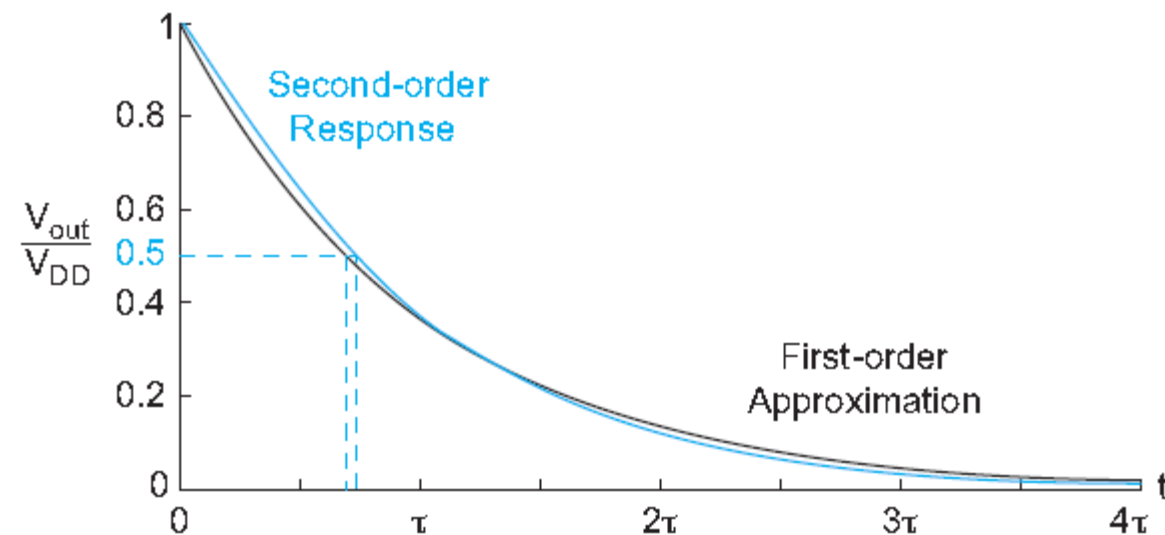
# Sometimes we can approximate the response considering just the dominant pole



- This works very well when the time constant of the dominant pole is much bigger than the other (error  $< 7\%$ )
- Worst case (when time constants are equal) has error  $< 15\%$
- The problem here is that this approximation doesn't describe well intermediate nodes
   
# Elmore Delay

- This approximation is based on finding an equivalent 1st – order response for the actual response of our circuit
- To find an equivalent  $\tau$  we match the area under the step response curve of our circuit to the area of a 1st-order response



$$\int_0^{\infty} V'_0 dt = \int_0^{\infty} V_0 dt = \sum RI = \sum RC \Delta V$$

# Elmore Delay


The Elmore time constant  $\tau_E$  is the sum over each node in the ladder of the resistance  $R_{n-1}$  between that node and the source  $V_{in}$ , multiplied by the capacitance on the node  $C_i$

$$t_{pd} = \tau_E * \ln 2$$

In this example, the  $\tau_D$  at  $V_{out}$  is calculated as

$$\tau_D = R_1 C_1 + (R_1 + R_2) C_2 + R_1 C_3$$

 
Note that  $R_3$  is dropped because it is not in the signal path ( $C_3$  gets connected directly to the node)



# Delay - Can we make this assumption?


- Conductor Resistance:

$$R = \frac{\rho L}{tW}$$

 

- Transistor resistance
  - Designer can set W and L
  - Actually  $I_{ds}^{-1}$
  - Prop<sup>-1</sup> to Vdd.
  - Approximated by:




$$R \approx \frac{L}{W} K_{technology}$$

 


# Delay - Capacitance

$C_{load}$  comes mainly from three factors:

   1. Gate capacitance of driven transistors.
2. Diffusion capacitance (due depletion region) of source/drain connected to the wire.
3. Wire capacitance.


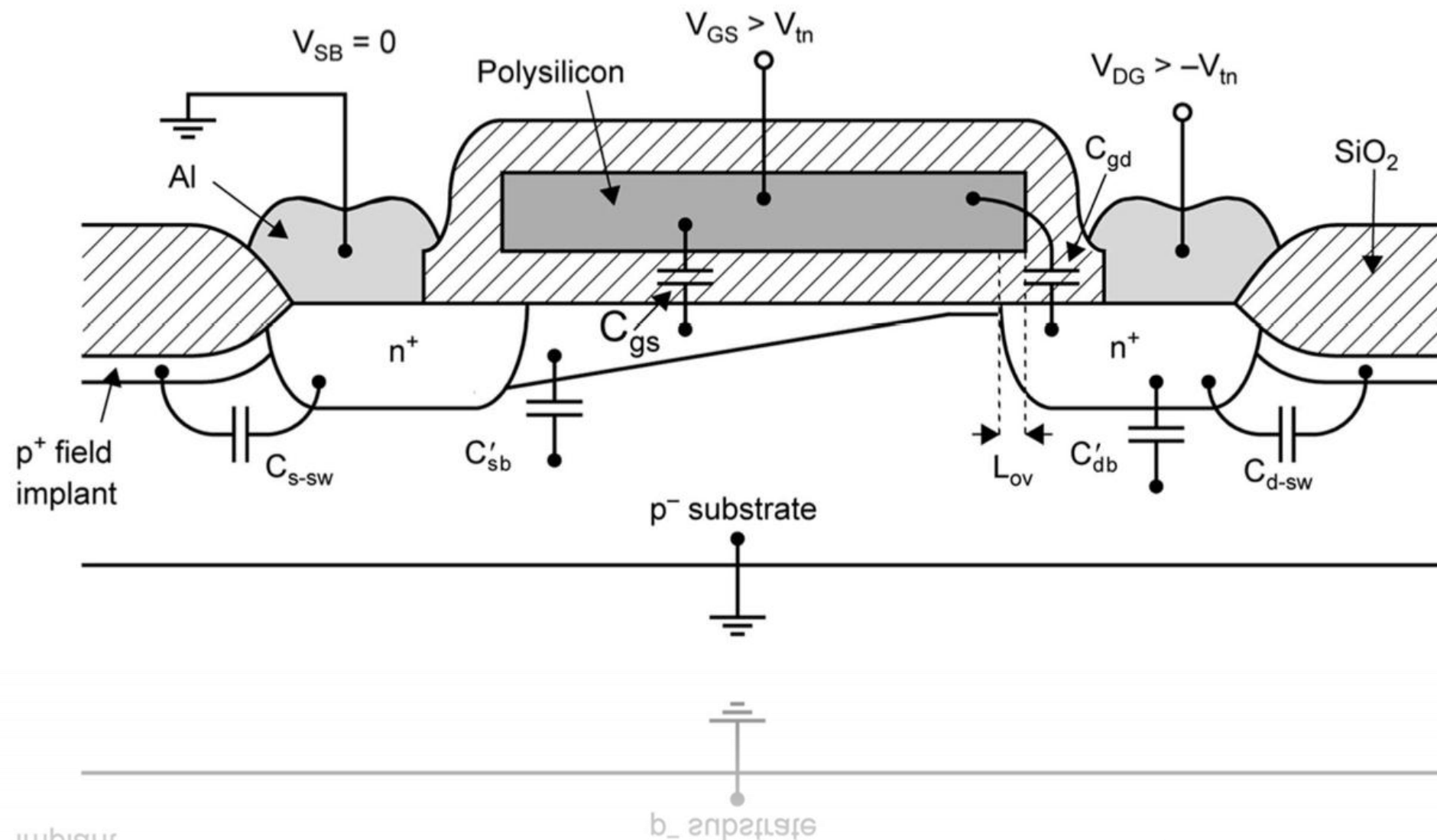
$$C_g = C_{ox}WL = C_{permicron}W, \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$



# Transistor Capacitance: Many Sources


# + Process Calibration

Pre Driver

Target


Load

Mille load

 

Delay 1

 We can adjust C to match Delay 1 with Delay 2



Having C, then R is just  $\text{Delay} / C \cdot \ln(2)$




# + Process Calibration

Find C iteratively until  
Delays match

$$t_{pdr} - t_{pdr\_cap}(C) = 0$$

$$t_{pdf} - t_{pdf\_cap}(C) = 0$$

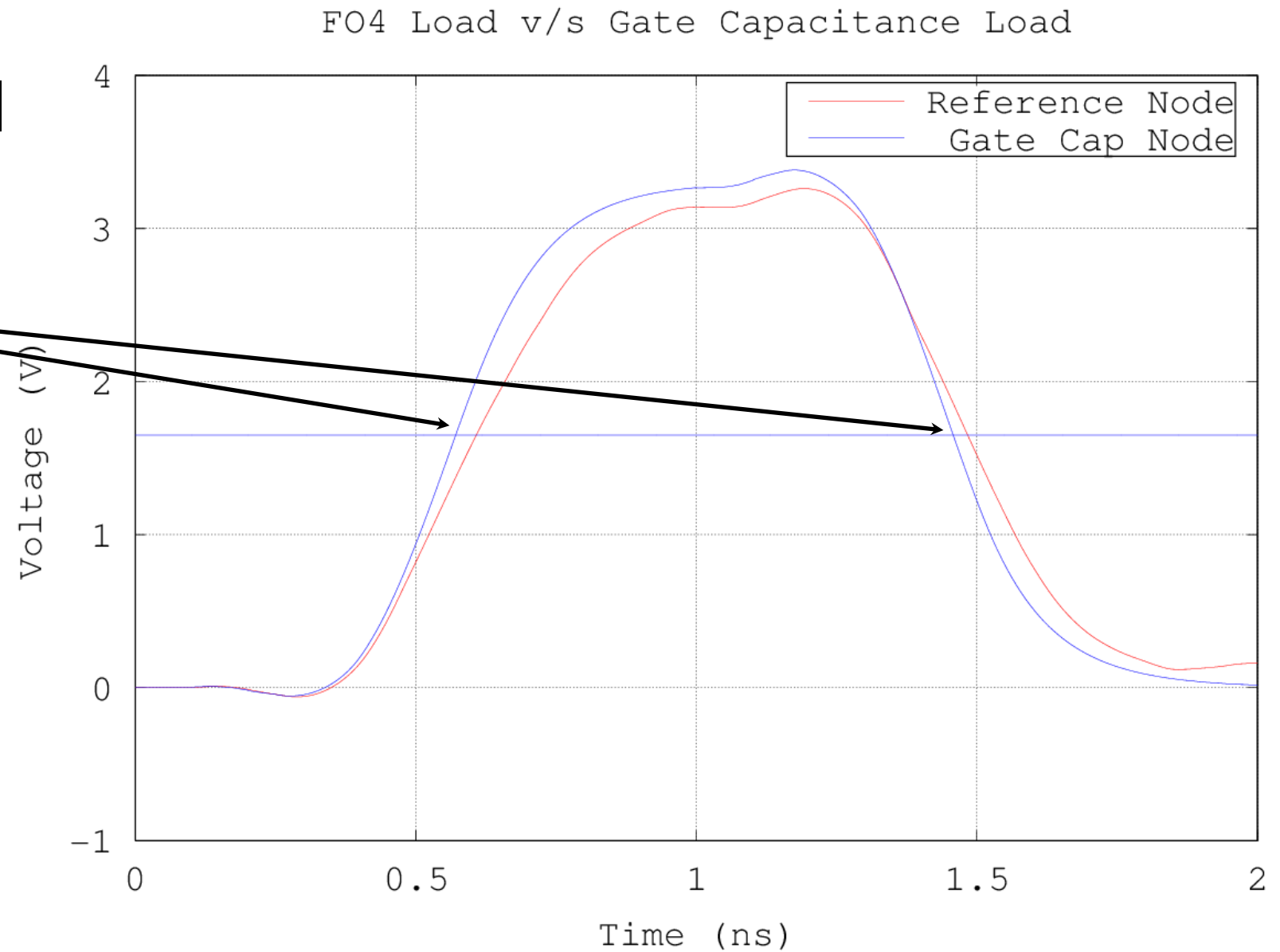


# Example

```
octave:1> source calib_opt.m
supply = 3.3000
cload_rise = 8.9632e-13
cload_fall = 7.6845e-13
cload = 8.3238e-13
WNDIFF_rise = 0.0015621
WNDIFF_fall = 0.0017749
WNDIFF = 0.0016685
delay = 2.6400e-10
cg = 1.4451e-15
Cdiff = 4.9887e-16
gamma = 0.23014
RN = 7321.1
RP = 1.4642e+04
Rsqu = 3.6605e+04
```

=====

 Cg = 1.445110 fF/um, Cd = 0.498875 fF/um Rsq = 36.605 kOhm/sq




Process	Cgate	Cdiff	Rsqu
0.5 um Pr05ocess	1.445 fF/um	0.499 fF/um	36.6 KOhm

\* [http://www.mosis.com/files/test\\_data/ami\\_c5n\\_corner\\_bsim3.txt](http://www.mosis.com/files/test_data/ami_c5n_corner_bsim3.txt)
 
# Current in a MOSFET

$$I_{ds} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$




\* Read Weste/Harris Ch3 for a complete derivation. Notice this is not even close to current in a real transistor.

# Gate Power
 
# What about Power?

- Well, Power = Energy / time
- And takes energy to move charges to a voltage source  
 $E = Q \text{ [cb]} * V \text{ [ J/cb ]}$
- Now to drive a gate we need  $C*\Delta V$  charges:  
 $E = C V^2$



$$E_{source} = \int_0^{T_c} i_{dd} V_{dd} dt = V_{dd} C_{load} \int_0^{T_c} \frac{dV_{dd}}{dt} dt = V_{dd} C_{load} \int_0^{V_{dd}} dV = C_{load} V_{dd}^2$$

$$E_C = \int_0^{T_c} i_C V_C dt = C \int_0^{T_c} V_C \frac{dV_C}{dt} dt = C_{load} \int_0^{V_{dd}} V_C dV = \frac{1}{2} C_{load} V_{dd}^2$$

$$E_{disipated} = E_{source} - E_C = \frac{1}{2} C_{load} V_{dd}^2$$

# Dynamic Power

- Now we know each **transition** dissipates some Energy:

$$E_{disipated} = \frac{1}{2} C_{load} V_{dd}^2$$

- Now, think about Power. How many times will a clock line take this Energy? Over which time?

$$P_{switching} = \frac{E}{T} = \frac{T f_{sw} (\frac{C_{load} V_{dd}^2}{2})}{T} = f_{sw} (\frac{C_{load} V_{dd}^2}{2})$$

- How many times does any signal transition per clock cycle? Let's say alpha.

$$P_{switching} = \alpha f_{sw} (\frac{C_{load} V_{dd}^2}{2})$$

# Leakage Power

- Transistor don't really shut down abruptly.
  - ▶ There is current even when  $V_{gs} < V_{th}$
  - ▶ So cells leak current and this depend on  $V_{th}$ :

$$I_{leak} = I_0 e^{\frac{V_{gs} - V_{th}}{nV_T}}$$

$$I_0 = I_{ds(V_{gs}=V_{th})}$$

\*Leakage can drop 10x for each 80mV of  $V_{th}$  at room  $t^0$

# Transition Probability

- Assume

- $P_{A=1} = 1/2$

- $P_{B=1} = 1/2$

- Then:

- $P_{Y=1} = 1/4$


- $P_{Y=0 \rightarrow 1} = P_{Y=0} * P_{Y=1} = 3/16$

- Analytic expression:

- $P_{Y=1} = (1 - P_{A=1})(1 - P_{B=1})$

- $P_{Y=0 \rightarrow 1} = P_{Y=0} P_{Y=1} = (1 - (1 - P_{A=1})(1 - P_{B=1}))(1 - P_{A=1})(1 - P_{B=1})$

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 





# Transition Probability

- Assume
  - $P_{A=1} = 1/2$
  - $P_{B=1} = 1/2$
- Then:
  - $P_{Y=1} = 1/2$
  - $P_{Y=0 \rightarrow 1} = P_{Y=0} * P_{Y=1}$
  - $\alpha_{0 \rightarrow 1} = 1/4$
- $P_1 = P_A(1-P_B) + P_B(1-P_A) = P_A + P_B - 2P_AP_B$
- $P_{0 \rightarrow 1} = P_0 P_1$   

$$= (1 - P_A + P_B - 2P_AP_B)(P_A + P_B - 2P_AP_B)$$

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

 

 


Reconvergence → Correlated inputs  
(NOT INDEPENDENT EVENTS)

$$P_Z = 1 - P_A * P(X/A) = 1$$

← Conditional Probability  
Probability of X provided A happens first

Reconvergent circuits quickly become hard to track and analyze

# Power Estimation - Example

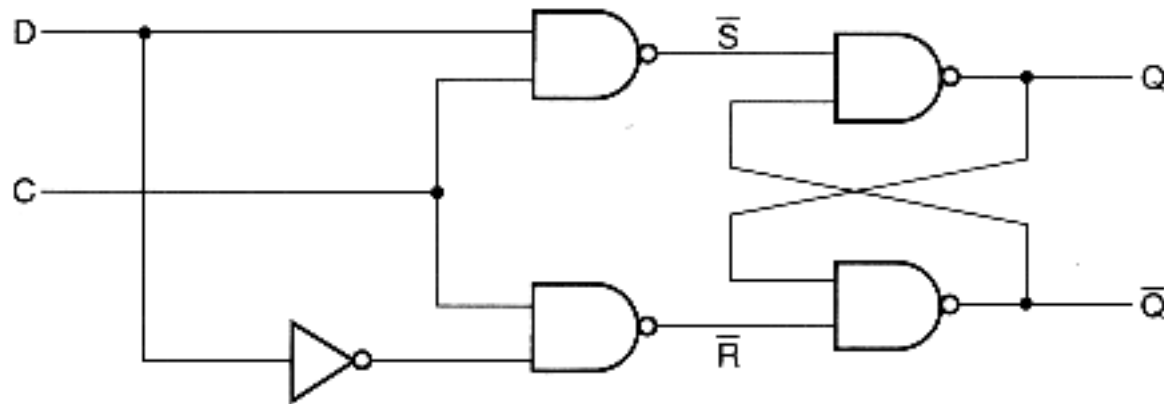


$$P = \frac{\alpha}{2} CV^2 f$$

Node	C	D	S'	R'	Q	Q'
Cycle 1	0	0	1	1	0	1
Cycle 1	1	1	0	1	1	0
Cycle 2	0	1	1	1	1	0
C						
Cycle 2	1	1	0	1	1	0
Transitions	2	1	2	0	1	1
Activity Factor	1	0.5	1	0	0.5	0.5

\* What if gates don't change instantly:

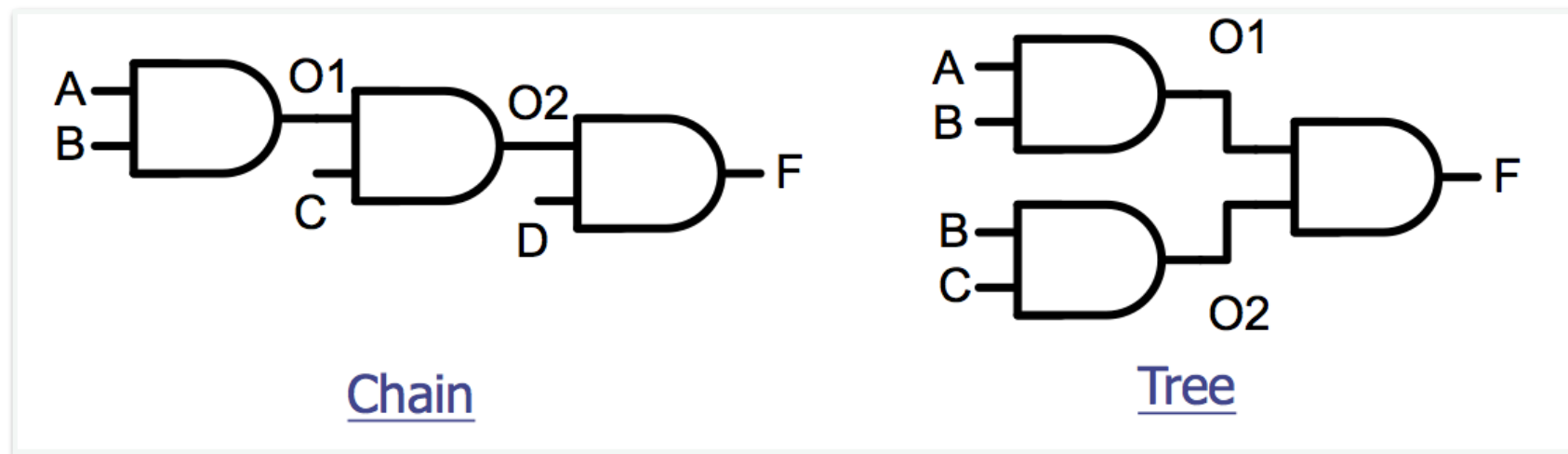
- Need to consider transient states too (hint: glitches)



Which has higher activity factor?  
(more in homework)
 
# +Crowbar current

- During circuit commutation both transistor may be active at the same time.
- On actual chips long transition time can make power dissipation to increase within 5-10% due crowbar current



Can add this 5-10% to your hand calculations


# System Analysis

# RC Delay model

- This model approximates the nonlinear transistor I-V and C-V characteristics with an average R and C
- Works well for delay estimation (not so well for analog behavior)
- Equivalent resistance R is the ratio  $V_{ds}/I_{ds}$  averaged across the switching interval of interest.
- A unit nMOS transistor is defined to have a resistance of R and gate and diffusion capacitances of C
- Transistors can be modeled based on the unit transistors



# Gate Performance

 


- Can you explain the transistor sizes?
- What is the value of  $C_{load}$ ?

$$I_{DS} = \frac{\mu C_{ox} W}{L} (V_{gs} - V_t)^2$$


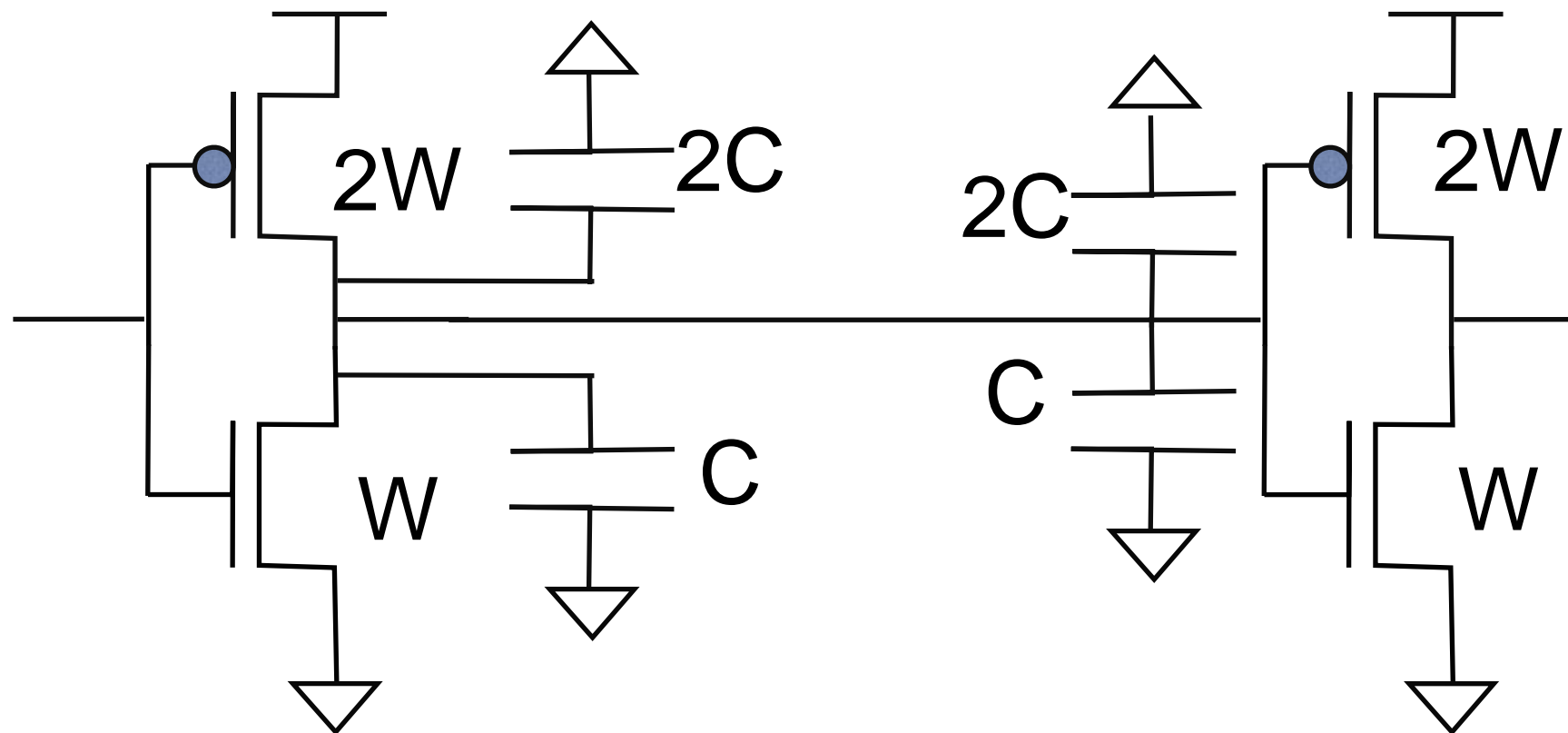
# Gate Performance

To perform delay analysis, we need to calculate R and C!



- Let's say that both  $C_g$  and  $C_{diff}$  are proportional to  $W$

$$C_g = C_{g,cons}W$$

$$C_{par} = C_{p,cons}W$$

- Resistance can be approximated to

$$R = \frac{W}{L} R_{sq}$$

# Sizing for minimum delay

- Wider transistors reduce  $R$  ( $R = \frac{L}{W} R_{sq}$ ), thus delay (RC) should decrease. Right?
- Wait a second... What about  $C_g = C_{g,cons} W$ ?

Will also grow, making the previous gate slower!

# Modelling inverter delay

$$t_{inv} = R_{drive}(C_{par} + C_{load})$$

$$C_{in} = 3WC_g$$

$$C_{par} = \gamma C_{in} \frac{L}{W}$$


$$R_{drive} = R_{sq} \frac{L}{W}$$

$$t_{inv} = R_{drive} C_{in} \left( \frac{C_{par}}{C_{in}} + \frac{C_{load}}{C_{in}} \right)$$


- Some algebra and...

$$t_{inv} = 3R_{sq}C_g \left( \gamma + \underbrace{\frac{C_{load}}{C_{in}}}_{\text{Fanout}} \right)$$

Fanout

 

# Optimizing an inverter chain

 

$$TotalDelay = \sum_{j=1}^N \tau_{inv} \left( \gamma + \frac{C_{in}^{j+1}}{C_{in}^j} \right)$$

$$\tau_{inv} = 3R_g C_g$$

\* How can we find optimum?

# Optimizing an inverter chain


$$\frac{d}{dC_{in}^j} Delay = \tau_{inv}\left(\frac{1}{C_{in}^{j-1}}\right) - \tau_{inv}\left(\frac{C_{in}^{j+1}}{(C_{in}^j)^2}\right)$$

When equal to zero:

$$C_j = \sqrt{C^{j+1} * C^{j-1}}$$

Or
 
$$\frac{C_{in}^j}{C_{in}^{j-1}} = \frac{C_{in}^{j+1}}{C_{in}^j}$$



At the optimum, each inverter does the same effort!

# If all do the same effort, how much then?

- Let's say at the optimum  $f$  is the fanout of every gate. If we multiply all the fanouts, we have

$$f = \sqrt[N]{\frac{C_2 C_3 \dots C_{N+1}}{C_1 C_2 \dots C_N}}$$


$$N = \frac{\ln\left(\frac{C_{out}}{C_{in}}\right)}{\ln(f)}$$

- On the other hand, at the optimum we have

$$TD = \sum_{j=1}^N \tau_{inv} \left( \gamma + \frac{C_{in}^{j+1}}{C_{in}^j} \right) = N \tau_{inv} (\gamma + f)$$

$$TD = \ln \left( \frac{C_{out}}{C_{in}} \right) \tau_{inv} \frac{(\gamma + f)}{\ln(f)}$$
 
# If all do the same effort, how much then?



To find the optimum, we derive  
 $TD$  with respect to  $f$

$$TD = \ln \left( \frac{C_{out}}{C_{in}} \right) \tau_{inv} \frac{(\gamma + f)}{\ln(f)}$$


This is done graphically...

**Optimum at roughly  $f = 4$  (FO4)**
 
# But in reality...

Circuits are not made of inverters only

$$\begin{array}{l} \tau_{j-1} \neq \tau_j \neq \tau_{j+1} \dots \\ \gamma_{j-1} \neq \gamma_j \neq \gamma_{j+1} \dots \end{array}$$



At optimum

$$\tau_{nand} f_{nand} = \tau_{inv} f_{inv}$$

$$\tau_{nand} \frac{C_j}{C_{j-1}} = \tau_{inv} \frac{C_{j+1}}{C_j}$$

Note that now fanouts are not equal, they depend on  $\tau$

To optimize a heterogeneous chain, we normalize by  $\tau_{inv}$

Keep an eye on this term  $\dashrightarrow$

$$\frac{\tau_{nand}}{\tau_{inv}} \frac{C_j}{C_{j-1}} = \frac{\tau_{inv}}{\tau_{inv}} \frac{C_{j+1}}{C_j}$$



# Logical Effort

$$LE_{gate} = \frac{\tau_{gate}}{\tau_{inv}} = \frac{C_{in,gate} R_{drive,gate}}{C_{in,inv} R_{drive,gate}}$$

If we normalize the fanout equation at optimum, it becomes:

$$\tau_{nand} \frac{C_j}{C_{j-1}} = \tau_{inv} \frac{C_{j+1}}{C_j} \Leftrightarrow LE_{nand} \frac{C_j}{C_{j-1}} = LE_{inv} \frac{C_{j+1}}{C_j}$$

Note that by definition  $LE_{inv} = 1$

***LE* of a logic gate tells how much more slowly the gate will drive a load compared to an inverter**

# Delay with Logical Effort

If we remember,:

$$TD = \sum_{j=1}^N \tau_j \left( \gamma + \frac{C_{in}^{j+1}}{C_{in}^j} \right)$$

Normalizing by  $\tau_{inv}$ :

$$TD_{norm} = \sum_{j=1}^N LE_j \left( \gamma + \frac{C_{in}^{j+1}}{C_{in}^j} \right)$$




Then, deriving and equaling to 0, at optimum we have

$$LE_1 \frac{C_2}{C_1} = LE_2 \frac{C_3}{C_2} = \dots = LE_{N-1} \frac{C_N}{C_{N-1}} \quad \text{Stage Effort (SE)}$$

We can calculate the *Effective Fanout* as

$$f_{eff} = \sqrt[N]{\prod_{j=1}^N LE_j \frac{C_{in,j+1}}{C_{in,j}}} = \sqrt[N]{\frac{C_{in,N}}{C_{in,1}} \prod_{j=1}^N LE_j} \quad \begin{array}{l} \text{Path Logical Effort (LE}_{path}\text{)} \\ \text{Path Fanout (f}_{path}\text{)} \end{array}$$

# Sizing - Example

   

How do we size?




Is LE equal for every output?

Hint: We want falling and rising times to be equal  
Also, rising and falling times should match inverter times

$$C_g = C_{g,cons} W$$

$$R = \frac{W}{L} R_{sq}$$

# Sizing - Example

   


How do we size?

Is LE equal for every output?

Hint: We want falling and rising times to be equal

Also, rising and falling times should match inverter times

# Optimizing Path Delay Example

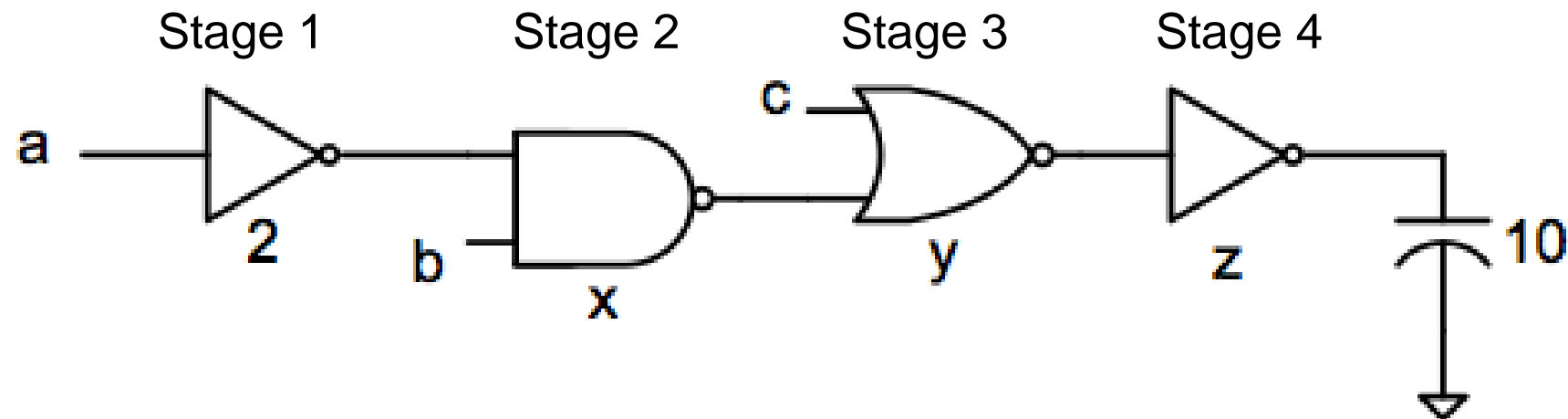

Stage	1	2	3	4	
LE	1	4/3	5/3	1	$LE_{path} = 2.2$
Fanout	$x/2$	$y/x$	$z/y$	$10/z$	$f_{eff} = 1.8$
Size	2	3.6	4.86	5.25	

$$SE = f_{eff}$$

$$LE_j \frac{C_{j+1}}{C_j} = f_{eff}$$

$$\sqrt[4]{\frac{10}{2} * 2.2} = 1.8$$

$$\frac{x}{2} \cdot 1 = 1.8$$



$$\frac{y}{x} \cdot \frac{4}{3} = 1.8$$

...
  
# Change Topology so effective fanout is closer to 4

$$f = a + \bar{b}a = \overline{\overline{c + b + \bar{a}}}$$

$$f = \overline{(c + b) \cdot a} = \bar{c}\bar{b}a$$



$$LE_{3\text{-input\_NAND}} = 5/3$$

$$LE_{path} = 1 * \frac{5}{3} = 1.66$$

$$f_{eff} = \sqrt{1.66 * \frac{10}{2}} = 2.88$$

**Better!**

# Review: To Size a Path

1. Find Effective Fanout

$$f_{eff} = \sqrt[N]{\frac{C_{in,N}}{C_{in,1}} \prod_{j=1}^N LE_j} = \sqrt[N]{f_{path}}$$

2. Estimate optimal number of stages. We want  $f_{eff}$  to be close to 4 at optimum

$$\widehat{f_{eff}} = 4 = \sqrt[\hat{N}]{f_{path}} \Leftrightarrow \hat{N} = \log_4(f_{path})$$

3. Re-implement using  $\hat{N}$  stages. Re-calculate  $LE_{path}$  and  $f_{eff}$
4. Calculate sizes, start from either end


$$LE_j \frac{C_{in,j+1}}{C_{in,j}} = f_{eff}$$


 
# LE Energy Considerations

$$-\frac{\partial E / \partial W_i}{\partial D / \partial W_i} = -\frac{\partial E / \partial C_i}{\partial D / \partial C_i} \cdot \frac{\partial C_i / \partial W_i}{\partial C_i / \partial W_i} = -\frac{ec_i / C_i}{\tau \cdot \left( \frac{1}{C_{i-1}} - \frac{C_{i+1}}{C_i^2} \right)} = \frac{ec_i}{\tau \cdot (h_{eff_i} - h_{eff_{i-1}})}$$

Bigger cells give less performance per energy spent.  
If we want to equalize marginal cost, then **BIG** cells should have **HIGHER** fanout.






# Notes on:

 
## *The Cost of Wires*

- Characterized by R & C  
(Oversimplified approximation)

$$R_w = \frac{\rho}{tW} \times L \quad C_w = \frac{\epsilon t}{d} \times L$$



- But propagation follows pi-model

 

$$Delay = \frac{1}{2} R_w C_w$$

- **$R \propto L, C \propto L \Rightarrow Delay \propto L^2$**

Using optimally spaced repeaters we can make it  $\propto L$

# Summary

- Delay is proportional to  $\ln(2) \cdot RC$ .
- Power can be dynamic ( $P = \frac{a}{2} C V^2 \times f$ ) and static ( $I_{leak} \cdot V_{dd}$ ).
- $C$  is load + parasitic.
- Optimum chain delay require equalized effective fanout.

# References

- Weste, Harris - CMOS VLSI Design 4th Edition
- Rabaey, Digital Integrated Circuits
- Sutherland, Sproull, Harris - Logical Effort: Designing Fast CMOS Circuits
- Kahng, Lienig, Markov, Hu - VLSI Physical Design: “From Graph Partitioning to Timing Closure”