

Verilog LAB I



Lab 1 – 1 bit full adder

- Use Karnaugh Map to derive logic expression for the addition.
- Create the file OneBitAdder.v
 - Write the Verilog code that implements binary addition operation based on the expression obtained previously
- Use the following interface

```
1 module onebitadder (  
2     input  a, b, cin,  
3     output sum, cout  
4 );
```

<i>a</i>	<i>b</i>	<i>cin</i>	<i>sum</i>	<i>cout</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Lab 2 – Basic modules

- This lab will consist on creating some basic designs (modules).
- A description of the design functionality will be provided.
- The objective is to translate the description into a synthesizable Verilog code.
- It is very important to use the module interface that will be provided.
- In order to do a syntax check on the Verilog code written, **vlogan** tool can be used. The following line can be executed on the shell


```
vlogan <verilog_file.v> -full64 -sverilog +v2k
```

Lab 2a – Parameterized 4-input MUX

- Write the Verilog code that implements a 4-input multiplexer (mux) with variable (parameterized) input and output bus width.

- Use the following interface


```
1 module mux4 #(
2     parameter WIDTH= 8
3 ) (
4     input  [WIDTH-1:0] din1, din2, din3, din4,
5     input  [1:0]       select,
6     output [WIDTH-1:0] dout
7 );
```

 

Lab 2b – Parameterized Register Bank

- Write the Verilog code that implements a D-type Register Bank with parameterized depth. It should:
 - Operate on positive edge of the clock (clk)
 - Have a Synchronous reset (rst)
 - Have an enable signal (wr_en) which allows data capturing only when asserted.
- Use the following interface

```
1 module register_bank #(
2     parameter WIDTH = 8
3 ) (
4     input  [0:0]      clk,
5     input  [0:0]      rst,
6     input  [0:0]      wr_en,
7     input  [WIDTH-1:0] in,
8     output [WIDTH-1:0] out
9 );
```

 


Lab 2c – Basic ALU

- Write the Verilog code for a basic ALU module (Arithmetic Logic Unit).
 - This ALU has to have addition, subtraction, multiplication and division operations.
 - It should have two variable (parameterized) width inputs and output bus in accordance.
 - Signal **zero**[0] should be asserted when the result of the current operation is 0.
 - Signal **error**[0] should be asserted when dividing by 0 is attempted or when input data is **not** valid.
 - On error condition, output must be forced to be -1
 - Operations should be described using Verilog arithmetic operators.

- Use the following interface
 
```
1 module ALU #(
2     parameter WIDTH = 8
3 ) (
4     input  [WIDTH-1:0]  in1, in2,
5     input  [3:0]        op,
6     input  [0:0]        nvalid_data,
7     output [2*WIDTH-1:0] out,
8     output [0:0]        zero,
9     output [0:0]        error
10 );
```



Thank You

