

Verilog LAB II



Lab 3 - Simulation


- This lab will be focused on simulating each module created in Lab 2 (a, b, c)
 - Simulations will be done using VCS tool.
- For lab 2a (Multiplexer) there is a test bench available, so the task is to simulate the module using that test bench.

```
vcs -full_debug -sverilog mux4_tb.v <verilog_file.v>
```

- For labs 2b and 2c:
 - Write a test bench for each module.
 - Simulate them in VCS.

Lab 4 – Full design

- The objective is to create a basic multicycle processor as shown in the diagram below.
 - Modules previously designed should be used. (Mux, ALU, Regbank)

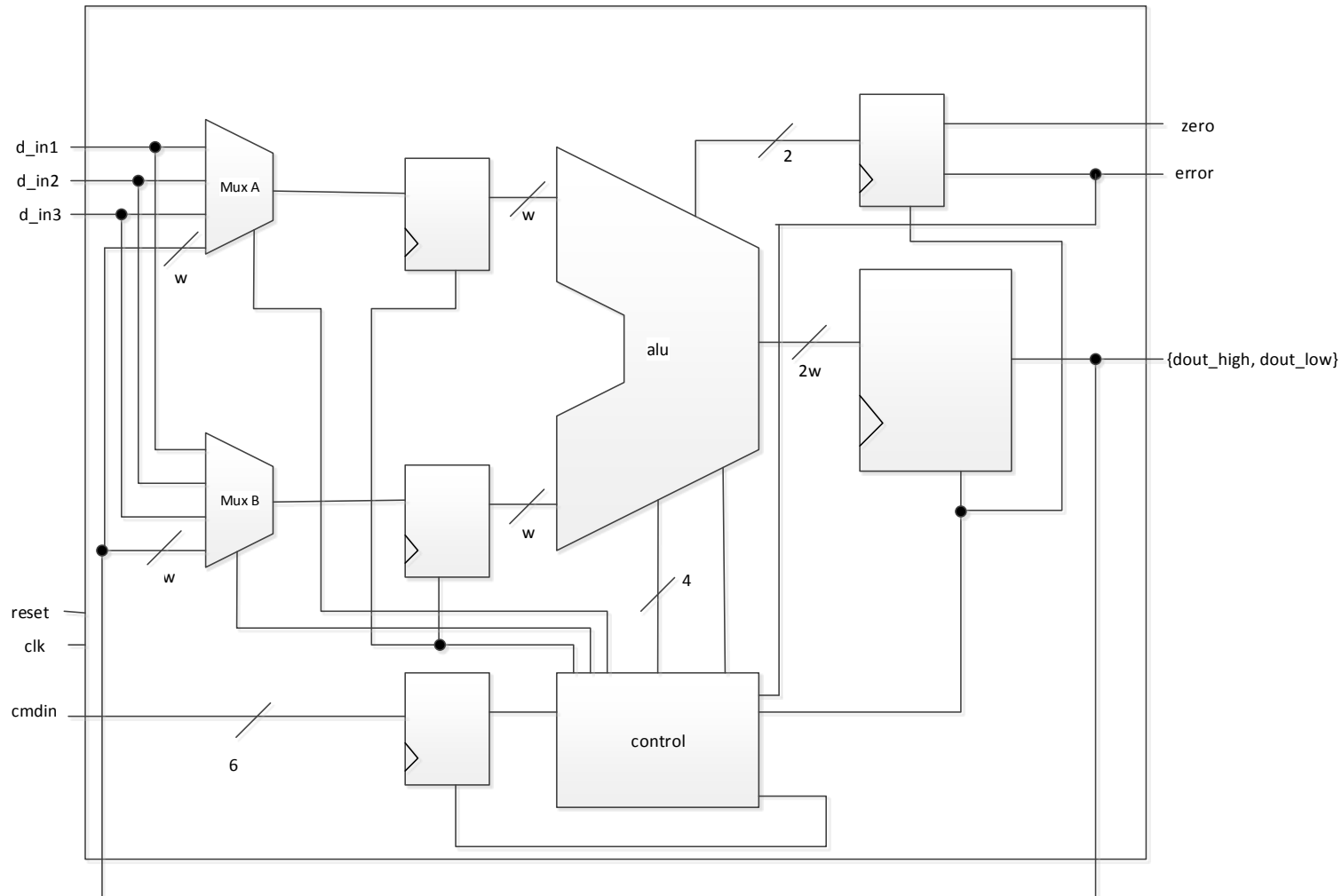


Lab 4 – Full design (cont.)

- Specifications of the design:
 - This is a multicycle processor (3 stages) with no pipelining.
 - It has 3 variable width input buses to be used as operands.
 - The **ALU** has 2 multiplexed inputs:
 - Each **MUX** is feed by the 3 input buses and the **ALU** output.
 - Details on how to control the **ALU** are available in Lab 2d.
 - Both reset (**rst**) and clock (**clk**) signals should be connected to every module that uses them.
 - It has a control unit feed by a 6 bit word (**cmdin**). This control unit has to:
 - Enable the register stages only when applicable
 - Select the outputs of each **MUX**
 - Provide the control signals for the **ALU**.
 - Inverted valid data signal must be asserted when data is feed from the feedback loop and the previous result was not valid (**Error** condition)
 - **OPCODE** to select the operation performed by the **ALU**.

Lab 4 – Full design (cont.)

 - The **control** block shall be designed to implement the following Instruction Set Architecture (ISA):



- The **opcode** bus should be decoded according to the following table:

opcode[1]	opcode[0]	Operation
0	0	Add
0	1	Sub
1	0	Mul
1	1	Div

Lab 4 – Full design (cont.)

- The control module

- Write the Verilog code for implementing this module based on the details and ISA provided previously.
- A test bench to validate this module. It should cover all possible operations, corner cases and exercise all outputs.
- Its interface should be as follows:

```
1 module control (  
2     input wire    [0:0]    clk,  
3     input wire    [0:0]    rst,  
4     input wire    [5:0]    cmd_in,  
5     input wire    [5:0]    p_error,  
6     output reg    [0:0]    aluin_reg_en,  
7     output reg    [0:0]    datain_reg_en,  
8     output reg    [0:0]    aluout_reg_en,  
9     output reg    [0:0]    nvalid_data,  
10    output wire    [1:0]    in_select_a,  
11    output wire    [1:0]    in_select_b,  
12    output reg    [4:0]    opcode  
13 );
```

Lab 4 – Full design (cont.)

- Full design

- Write the Verilog code that implements this simple microprocessor. At this point it is mostly about connecting together all the modules created so far.
- A test bench will be provided.
- Its interface should be as follows

```
1  module top #(
2      parameter WIDTH= 8
3  ) (
4      input wire    [0:0]  clk,
5      input wire    [0:0]  rst,
6      input wire    [5:0]  cmdin,
7      input wire    [WIDTH-1:0]  din_1,
8      input wire    [WIDTH-1:0]  din_2,
9      input wire    [WIDTH-1:0]  din_3,
10     output wire   [WIDTH-1:0]  dout_low,
10     output wire   [WIDTH-1:0]  dout_high,
10     output wire   [0:0]  zero,
10     output wire   [0:0]  error
11 );
```

Thank You

